

Soluciones Tema 2

Ejercicio 1.

$$Y = (\overline{A+B})\overline{C} + \overline{C}D$$

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio1 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio1;

architecture arquitectural of Ejercicio1 is

begin

y<='0' when (C='1') else (A nor B) or D;

end arquitectural;
```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Ejercicio1 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio1;

architecture arquitectura2 of Ejercicio1 is

begin

y<= '1' when (A&B&C&D="000-")else
    '1' when (A&B&C&D="0101")else
    '1' when (A&B&C&D="1001")else
    '1' when (A&B&C&D="1101")else
    '0';

end arquitectura2;
```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio1 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio1;

architecture arquitectura2 of Ejercicio1 is

begin

y<= not C when (D='1') else not(A or B or C);

end arquitectura2;
```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio1 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio1;

architecture arquitectura2 of Ejercicio1 is


begin

y<= '1' when ((A='0' and B='0' and C='0')or (C='0' and D='1')) else '0';

end arquitectura2;
```

Ejercicio 2.

(a)

 

(b)

$$S0 = \overline{B} \cdot \overline{C} + \overline{A} \cdot B$$

$$S1 = \overline{A} + \overline{B} \cdot C + B \cdot \overline{C}$$

(c)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio2 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          S0 : out STD_LOGIC;
          S1 : out STD_LOGIC);
end Ejercicio2;

architecture architectural of Ejercicio2 is

begin

    S0<= (B nor C) when (A='1') else (B or (not c));
    S1<= '1' when (A='0') else B xor C;

end architectural;
```

Ejercicio 3.

(a)

$$Y = A \cdot \overline{B} \cdot \overline{D} + B \cdot D$$

$$Y = (A + B)(\overline{B} + D)(\overline{A} + \overline{D})$$

$$Y = (B + \overline{D})(\overline{B} + D) \cdot (A + D) = (A + B)(\overline{B \oplus D})$$

$$Y = (B + \overline{D})(A + D)(\overline{A} + \overline{B})$$

$$Y = (A + B)(\overline{B} + D)(B + \overline{D}) = (A + B)(\overline{B \oplus D})$$

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_1 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio3_1;

architecture arquitectural of Ejercicio3_1 is

begin

    y<= (B and D) or (A and (not B) and (not D));

end arquitectural;
```

(b)

A partir del mapa de karnaugh

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_2_2 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio3_2_2;

architecture arquitectura2 of Ejercicio3_2_2 is

begin

    Y<= '1' when (A='0' and B='1' and C='1' and D='1') or (A='1' and B='0' and
    C='1' and D='0') else
    '-' when (C='0' and (A='1' or B='1' or D='1')) or (A='1' and B='1' and
    C='1' and D='1') else
    '0';

end arquitectura2;
```

Otra posibilidad a partir del mapa de karnaugh

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_2_2 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio3_2_2;

architecture arquitectura2 of Ejercicio3_2_2 is
    signal entrada : std_logic_vector (3 downto 0);
begin
    entrada<=A&B&C&D;

    Y<= '1' when (entrada="0111" or entrada="1010") else
        '0' when (entrada="0000" or entrada="001-" or entrada="-110" or
            entrada="1011") else
        '-';
end arquitectura2;
```

Otra posibilidad a partir de la primera ecuación del apartado a)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_2 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out  STD_LOGIC);
end Ejercicio3_2;

architecture arquitectura2 of Ejercicio3_2 is
begin
    Y<= (A and (not D)) when (B='0') else D;

end arquitectura2;
```

Otra posibilidad sería a partir de la primera ecuación del apartado a)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_2 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio3_2;

architecture arquitectura2 of Ejercicio3_2 is
begin

    Y<= B when (D='1') else (A and (not B));

end arquitectura2;
```

(c)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_3 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio3_3;

architecture arquitectura3 of Ejercicio3_3 is
    signal entrada : std_logic_vector (3 downto 0);
begin
    entrada<=A&B&C&D;
    with entrada select

        Y<='0' when "0000",
          '0' when "001-",
          '0' when "0110",
          '0' when "1110",
          '0' when "1011",
          '1' when "0111",
          '1' when "1010",
          '-' when others;

end arquitectura3;
```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio3_3 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejercicio3_3;

architecture arquitectura3 of Ejercicio3_3 is
    signal entrada : std_logic_vector (3 downto 0);
begin
    entrada<=A&B&C&D;
    with entrada select

        Y<='0' when "0000"|"001-"|"0110"|"1110"|"1011",
            '1' when "0111"|"1010",
            '-' when others;

end arquitectura3;
```

Ejercicio 4.

(a)

$$Y = B \cdot C + A \cdot C + A \cdot B$$

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejemplo4 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejemplo4;

architecture arquitectura3 of Ejemplo4 is

begin

    y<= (B and C) or (A and C) or (A and B);

end arquitectura3;
```

```

(b) library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Ejemplo4 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejemplo4;

architecture arquitectural_1 of Ejemplo4 is

begin

    y<= B or C when (A='1') else B and C;

end arquitectural_1;

```

Lo mismo de antes se puede hacer con las otras dos variables, es decir:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejemplo4 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejemplo4;

architecture arquitectural_1 of Ejemplo4 is

begin

    y<= A or C when (B='1') else A and C;

end arquitectural_1;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejemplo4 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          Y : out STD_LOGIC);
end Ejemplo4;

architecture arquitectural_1 of Ejemplo4 is

begin

    y<=A or B when (C='1') else A and B;

end arquitectural_1;

```



```

(c) library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Ejemplo4 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          Y : out  STD_LOGIC);
end Ejemplo4;

architecture arquitectural of Ejemplo4 is

    signal entrada : std_logic_vector (2 downto 0);

begin
    entrada<=A&B&C;
    with entrada select

        y<= '1' when "11-",
            '1' when "011",
            '1' when "101",
            '0' when others;

end arquitectural;

```

Ejercicio 5.(a)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Ejercicio5_1 is
    Port ( M1 : in  STD_LOGIC;
          M2 : in  STD_LOGIC;
          M3 : in  STD_LOGIC;
          M4 : in  STD_LOGIC;
          TA : out  STD_LOGIC;
          MA : out  STD_LOGIC;
          I  : out  STD_LOGIC;
          MR : out  STD_LOGIC);
end Ejercicio5_1;

architecture arquitectural of Ejercicio5_1 is

begin
    TA <= '1' when (M1&M2&M3&M4="1111") else '0';
    MA <= '1' when (M1&M2&M3&M4="0111" or M1&M2&M3&M4="1011" or
        M1&M2&M3&M4="1101" or M1&M2&M3&M4="1110" else
        '0';
    I  <= '1' when (M1&M2&M3&M4="0011" or M1&M2&M3&M4="0101" or
        M1&M2&M3&M4="0110" or M1&M2&M3&M4="1001" or M1&M2&M3&M4="1010" or
        M1&M2&M3&M4="1100") else
        '0';
    MR <= '1' when (M1&M2&M3&M4="000-" or M1&M2&M3&M4="0010" or
        M1&M2&M3&M4="0100" or M1&M2&M3&M4="1000" else
        '0';

end arquitectural;

```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio5_1 is
    Port ( M1 : in  STD_LOGIC;
          M2 : in  STD_LOGIC;
          M3 : in  STD_LOGIC;
          M4 : in  STD_LOGIC;
          TA : out STD_LOGIC;
          MA : out STD_LOGIC;
          I  : out STD_LOGIC;
          MR : out STD_LOGIC);
end Ejercicio5_1;

architecture architectural of Ejercicio5_1 is
begin

TA <= '1' when (M1='1' and M2='1' and M3='1' and M4='1') else
    '0';
MA <= '1' when (M1='0' and M2='1' and M3='1' and M4='1') else
    '1' when (M1='1' and M2='0' and M3='1' and M4='1') else
    '1' when (M1='1' and M2='1' and M3='0' and M4='1') else
    '1' when (M1='1' and M2='1' and M3='1' and M4='0') else
    '0';
I  <= '1' when (M1='0' and M2='0' and M3='1' and M4='1') else
    '1' when (M1='0' and M2='1' and M3='0' and M4='1') else
    '1' when (M1='0' and M2='1' and M3='1' and M4='0') else
    '1' when (M1='1' and M2='0' and M3='0' and M4='1') else
    '1' when (M1='1' and M2='0' and M3='1' and M4='0') else
    '1' when (M1='1' and M2='1' and M3='0' and M4='0') else
    '0';
MR<= '1' when (M1='0' and M2='0' and M3='0') else
    '1' when (M1='0' and M2='0' and M4='0') else
    '1' when (M1='0' and M3='0' and M4='0') else
    '1' when (M2='0' and M3='0' and M4='0') else
    '0';
end architectural;
```

(b)

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio5_2 is
    Port ( M1 : in  STD_LOGIC;
          M2 : in  STD_LOGIC;
          M3 : in  STD_LOGIC;
          M4 : in  STD_LOGIC;
          TA : out STD_LOGIC;
          MA : out STD_LOGIC;
          I  : out STD_LOGIC;
          MR : out STD_LOGIC);
end Ejercicio5_2;
```

```

architecture arquitectura2 of Ejercicio5_2 is
    signal entradas : std_logic_vector (3 downto 0);
    signal salidas : std_logic_vector (3 downto 0);

begin

    entradas<=M1&M2&M3&M4;
    with entradas select
        salidas <= "0001" when "000-",
                  "0001" when "0010",
                  "0001" when "0100",
                  "0001" when "1000",
                  "0100" when "0111",
                  "0100" when "1011",
                  "0100" when "1101",
                  "0100" when "1110",
                  "1000" when "1111",
                  "0010" when others;

        TA<=salidas(3);
        MA<=salidas(2);
        I<=salidas(1);
        MR<=salidas(0);

end arquitectura2;

```

Otra posibilidad

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio5_3 is
    Port ( entradas : in std_logic_vector (3 downto 0);
          salidas : out std_logic_vector (3 downto 0));
end Ejercicio5_3;

architecture arquitectura3 of Ejercicio5_3 is

begin

    with entradas select
        salidas <= "0001" when "000-",
                  "0001" when "0010",
                  "0001" when "0100",
                  "0001" when "1000",
                  "0100" when "0111",
                  "0100" when "1011",
                  "0100" when "1101",
                  "0100" when "1110",
                  "1000" when "1111",
                  "0010" when others;

end arquitectura3;

```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio5_3 is
    Port ( entradas : in std_logic_vector (3 downto 0);
          salidas  : out std_logic_vector (3 downto 0));
end Ejercicio5_3;

architecture arquitectura3 of Ejercicio5_3 is

begin

    with entradas select
        salidas <= "0001" when "000-"|"0010"|"0100"|"1000",
                  "0100" when "0111"|"1011"|"1101"|"1110",
                  "1000" when "1111",
                  "0010" when others;

end arquitectura3;
```

Otra posibilidad

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio5_4 is
    Port ( M1 : in  STD_LOGIC;
          M2 : in  STD_LOGIC;
          M3 : in  STD_LOGIC;
          M4 : in  STD_LOGIC;
          TA : out  STD_LOGIC;
          MA : out  STD_LOGIC;
          I  : out  STD_LOGIC;
          MR : out  STD_LOGIC);
end Ejercicio5_4;

architecture arquitectura4 of Ejercicio5_4 is
    signal entradas : std_logic_vector (3 downto 0);
begin

    entradas<=M1&M2&M3&M4;

    with entradas select
        TA <= '1' when "1111",
            '0' when others;

    with entradas select
        MA <= '1' when "0111",
            '1' when "1011",
            '1' when "1101",
            '1' when "1110",
            '0' when others;
```

```
with entradas select
    I <= '1' when "0011",
        '1' when "0101",
        '1' when "0110",
        '1' when "1001",
        '1' when "1010",
        '1' when "1100",
        '0' when others;

with entradas select
    MR <= '1' when "0000",
        '1' when "0001",
        '1' when "0010",
        '1' when "0100",
        '0' when others;

end arquitectura4;
```