

### Soluciones Tema 3

#### Ejercicio 1.

$$n \geq \frac{\log_{10}(x+1)}{\log_{10}(2)}$$

- a) 101011001b
- b) 100000000b
- c) 11111000011b
- d) 1011101001b

#### Ejercicio 2.

-Si el número finaliza en '1' será impar sino será par.

- a) 1001000110011101b  $\rightarrow 2^0+2^2+2^3+2^4+2^7+2^8+2^{12}+2^{15}=37277$
- b) 0111000111100011b  $\rightarrow 2^0+2^1+2^5+2^6+2^7+2^8+2^{12}+2^{13}+2^{14}=29155$
- c) 1111111100000110b  $\rightarrow 2^1+2^2+2^8+2^9+2^{10}+2^{11}+2^{12}+2^{13}+2^{14}+2^{15}=65286$
- d) 0011110011010110b  $\rightarrow 2^1+2^2+2^4+2^6+2^7+2^{10}+2^{11}+2^{12}+2^{13}=15574$

#### Ejercicio 3.

- a) 1001000110011101b  $\rightarrow$  110635o  $\rightarrow$  919Dh
- b) 0111000111100011b  $\rightarrow$  70743o  $\rightarrow$  71E3h
- c) 1111111100000110b  $\rightarrow$  177406o  $\rightarrow$  FF06h
- d) 0011110011010110b  $\rightarrow$  36326o  $\rightarrow$  3CD6h

#### Ejercicio 4.

$$-(2^{n-1}) \leq x \leq 2^{n-1} - 1 = -32768 \leq x \leq 32767$$

- a) 1053  $\rightarrow$  0000010000011101
- b) 4017  $\rightarrow$  0000111110110001
- c) -356  $\rightarrow$  1111111010011100
- d) -8950  $\rightarrow$  1101110100001010

#### Ejercicio 5.

-Si el bit de la izquierda es un '1' será un número negativo.

- a) 0001111001110101  $\rightarrow 2^0+2^2+2^4+2^5+2^6+2^9+2^{10}+2^{11}+2^{12}=7797$
- b) 1111111111111111  $\rightarrow 2^0+2^1+2^2+2^3+2^4+2^5+2^6+2^7+2^8+2^9+2^{10}+2^{11}+2^{12}+2^{13}+2^{14}-(2^{15})=-1$
- c) 0001100111100001  $\rightarrow 2^0+2^5+2^6+2^7+2^8+2^{11}+2^{12}=6625$
- d) 1111100000011100  $\rightarrow 2^2+2^3+2^4+2^{11}+2^{12}+2^{13}+2^{14}-(2^{15})=-2020$

**Ejercicio 6.**

I.

- a) -125 -> 10000011      c) 15 -> 00001111      e) 85 -> 01010101  
 b) 98 -> 01100010      d) -12 -> 11110100      f) -93 -> 10100011

II.

- a) b+e -> overflow      c) a-f      e) d-a

$$\begin{array}{r} 01100010 \\ + 01010101 \\ \hline 10110111 = -73 \end{array}$$

$$\begin{array}{r} 10000011 \\ + 01011101 \\ \hline 11100000 = -32 \end{array}$$

$$\begin{array}{r} 11110100 \\ + 01111101 \\ \hline 01110001 = 113 \end{array}$$

- b) e-d      d) b+c      f) a+d -> overflow

$$\begin{array}{r} 01010101 \\ + 00001100 \\ \hline 01100001 = 97 \end{array}$$

$$\begin{array}{r} 01100010 \\ + 00001111 \\ \hline 01110001 = 113 \end{array}$$

$$\begin{array}{r} 10000011 \\ + 11110100 \\ \hline 01110111 = 119 \end{array}$$

**Ejercicio 7.**

Se desea diseñar un sistema que realice la suma o la resta de dos números de 4 bits codificados en complemento a 2. La operación realizada por el circuito será función de una variable lógica denominada R: R=1 operación de resta, R=0 operación de suma. Las salidas del sistema serán por un lado cuatro bits correspondientes al resultado de la operación, y por otro un bit más que tomará el valor 1 si se produce overflow al realizar la operación. La Fig. 1 representa las entradas y salidas del sistema.


 



Figura 1 . Definición del sistema lógico a diseñar

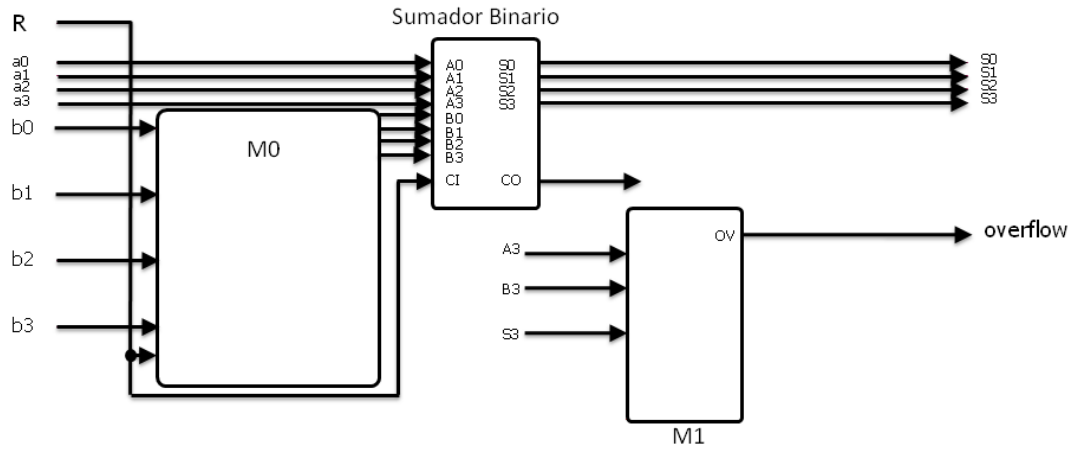- a) Implementación del sistema utilizando un sumador binario de dos números de 4 bits y las puertas lógicas que se consideren oportunas.



- M0: Si R='1' Cálculo del complemento a 1,  
 $B0 = \overline{b0}$ ,  $B1 = \overline{b1}$ ,  $B2 = \overline{b2}$  y  $B3 = \overline{b3}$   
 Si R='0'  
 $B0 = b0$ ,  $B1 = b1$ ,  $B2 = b2$  y  $B3 = b3$

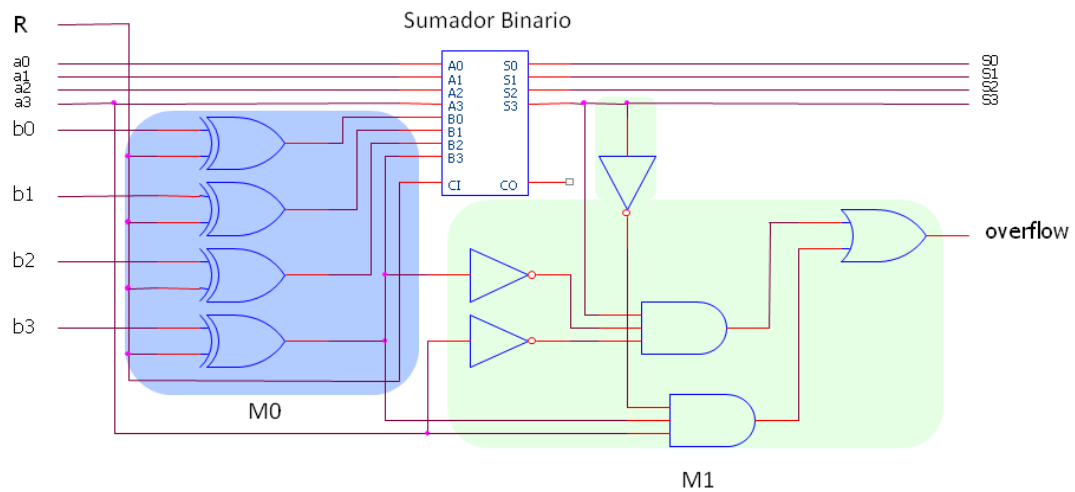- M1: Se activará la salida OV siempre que se produzca "overflow".



b)

c.1) a=1011b; b=1100b; R=1


```
  1011
+ 0100
-----
 1111 = -1  overflow='0'
```

c.2) a=1110b; b=1111b; R=0

```
  1110
+ 1111
-----
 1101 = -3  overflow='0'
```

### Ejercicio 8.

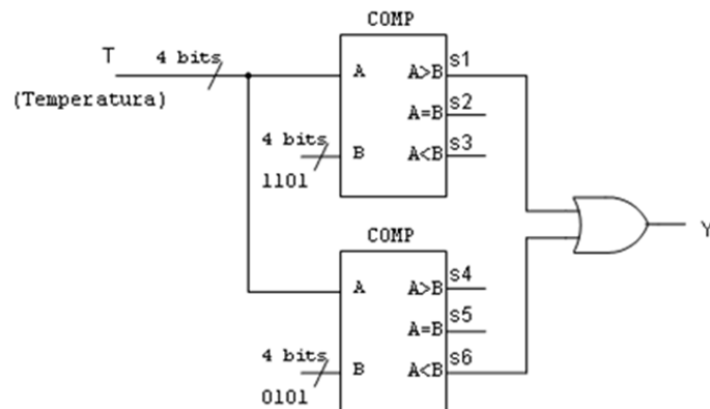- a) Tendremos que comparar la temperatura que nos proporciona el sensor, con los dos márgenes de temperatura, y si estamos dentro de dichos márgenes activaremos la salida del sistema. Recordar que los comparadores interpretarán los números presentes en la entrada como si estuvieran codificados en binario natural, pero en realidad están en complemento a 2, así que lo tendremos que tener en cuenta a la hora de obtener los dos umbrales de comparación.



b)

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_arith.all;
USE IEEE.std_logic_unsigned.all;
```

```
ENTITY Ejercicio_9 IS
```

```

        PORT (T: IN std_logic_vector(3 downto 0);
              Y: OUT std_logic);

END Ejercicio_9;

ARCHITECTURE Estructural OF Ejercicio_9 IS
    -- Declaración del componente COMPARADOR.
    COMPONENT Comparador_4bits IS
        PORT (A, B : IN std_logic_vector(3 downto 0);
              A_mayor, A_igual, A_menor : OUT std_logic);

    END COMPONENT;

    signal s1,s2,s3,s4,s5,s6 : std_logic; --Señales internas.

BEGIN
    U1: Comparador_4bits PORT MAP(A=>T,
                                  B=>"1101",
                                  A_mayor=>s1,
                                  A_igual=>s2,
                                  A_menor=>s3);

    U2: Comparador_4bits PORT MAP(A=>T,
                                  B=>"0101",
                                  A_mayor=>s4,
                                  A_igual=>s5,
                                  A_menor=>s6);

    Y<=s1 or s6;

END Estructural;

--Descripción del comparador de 4 bits

ENTITY Comparador_4bits IS
    PORT (A, B : IN std_logic_vector(3 downto 0);
          A_mayor, A_igual, A_menor : OUT std_logic);

END Comparador_4bits;

ARCHITECTURE comparador OF Comparador_2bits IS
BEGIN
    A_mayor<='1' WHEN (A>B) ELSE '0';
    A_igual<='1' WHEN (A=B) ELSE '0';
    A_menor<='1' WHEN (A<B) ELSE '0';
END comparador ;

```


### Ejercicio 9.

- a) 34,2344-> 1000100011110000
- b) 52,1878-> 1101000011000000
- c) 15,0625-> 0011110001000000


d) 60,7854-> 1111001100100100

**Ejercicio 10.**

 
a) 34,2344->01000010000010001111000000000110



 
b) 52,1878-> 01000010010100001100000001001110



 c) 15,0625-> 01000001011100010000000000000000




d) 60,7854-> 01000010011100110010010000111111

 

Ejercicio 11.

- El superíndice " ' " denota las entradas y salidas del multiplexor 16:1 a implementar.

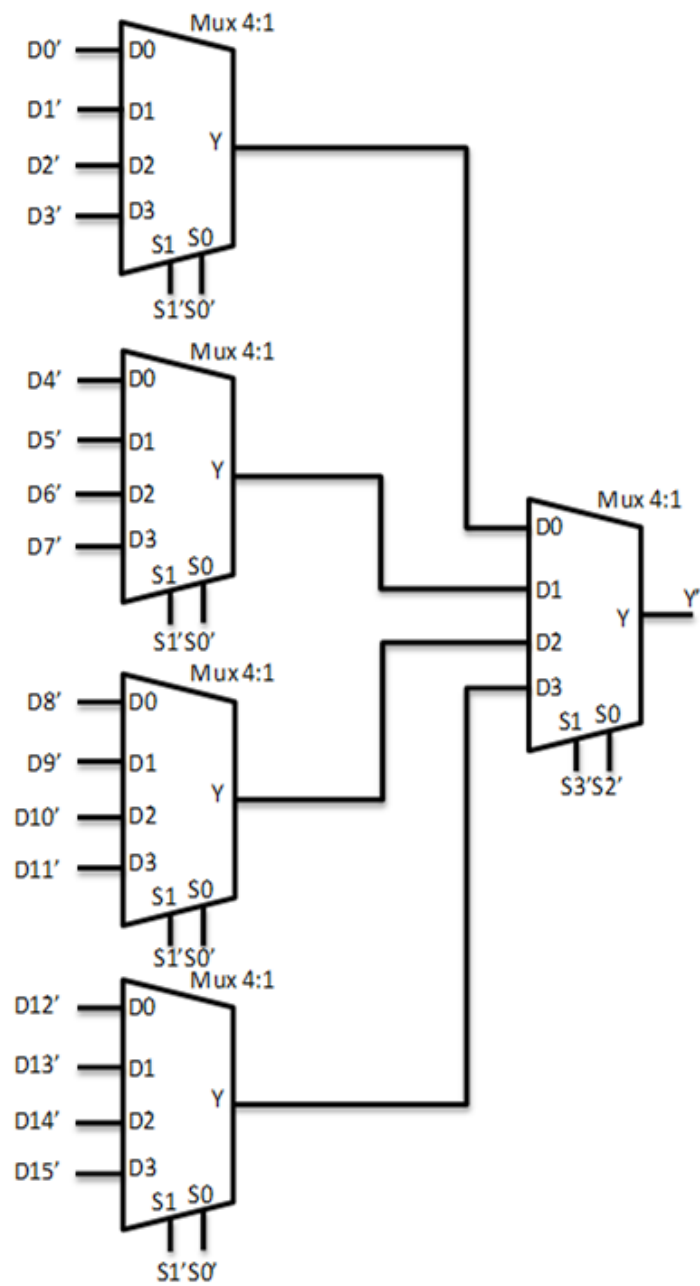

**Ejercicio 12.**

a)

I3	I2	I1	I0	O0	O1
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	1	0	1


b)

I3 I2	00	01	11	10	
I1 I0	00	0	0	0	0
01	1	1	1	0	
11	1	1	0	1	
10	1	0	0	0	

$$O0 = \bar{I3}\bar{I2}I1 + \bar{I2}I1I0 + I2\bar{I1}I0 + \bar{I3}I0$$



c)

 

d)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Ejercicio_13 is
    port(I3,I2,I1,I0 : in std_logic;
          O0,O1 : out std_logic);
end Ejercicio_13;

architecture Behavioral of Ejercicio_13 is


    signal entrada: std_logic_vector (3 downto 0);
begin
    entrada<=I3&I2&I1&I0;
    O0<=((not I3)and (not(I2) and I1) or ((not I2) and I1 and I0)
        or (I2 and (not I1) and I0) or ((not I3) and I0);

    O1<='1' when (entrada>9) else '0';

end Behavioral;
```


e)

I2	I1	I0	O1
0	0	0	0
0	0	1	0
0	1	0	I3
0	1	1	I3
1	0	0	I3
1	0	1	I3
1	1	0	I3
1	1	1	I3

 


OTRA POSIBLE SOLUCIÓN:

I3	I2	I1	O1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

f)

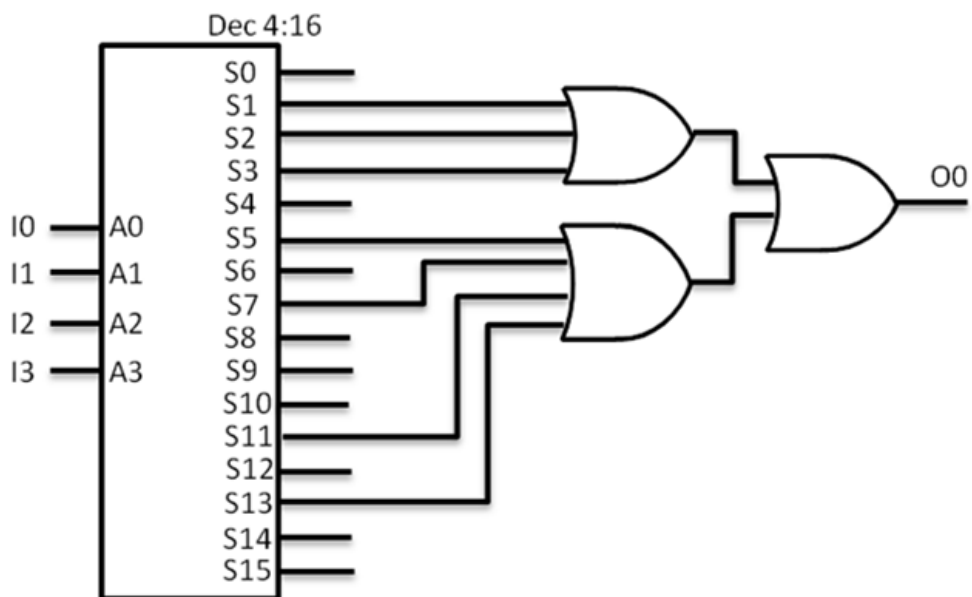

**Ejercicio 13.**

**a)**

d	c	b	a	y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

**b)**

e	y	X0	X1	X2	X3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$X0 = \bar{e}\bar{y}$$

$$X1 = \bar{e}y$$


$$X2 = e\bar{y}$$

$$X3 = ey$$

c)

e	y	g	f	X0	X1	X2	X3	S
0	0	0	0	1	0	0	0	1
0	0	0	1	1	0	0	0	0
0	0	1	0	1	0	0	0	0
0	0	1	1	1	0	0	0	0
0	1	0	0	0	1	0	0	0
0	1	0	1	0	1	0	0	1
0	1	1	0	0	1	0	0	0
0	1	1	1	0	1	0	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	0	0	1	0	0
1	0	1	0	0	0	1	0	1
1	0	1	1	0	0	1	0	0
1	1	0	0	0	0	0	1	0
1	1	0	1	0	0	0	1	0
1	1	1	0	0	0	0	1	0
1	1	1	1	0	0	0	1	1

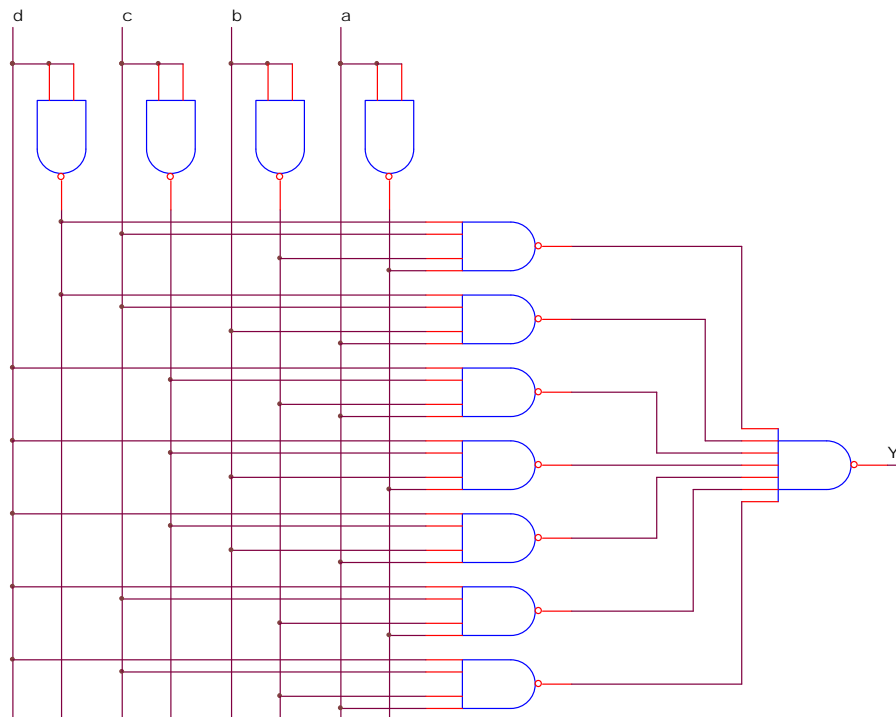d)  $y = \bar{d}\bar{c}\bar{b}\bar{a} + \bar{d}\bar{c}b\bar{a} + \bar{d}\bar{c}\bar{b}a + \bar{d}c\bar{b}\bar{a} + \bar{d}c\bar{b}a + d\bar{c}\bar{b}\bar{a} + d\bar{c}\bar{b}a$



e)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ejercicio_14 is
    port(g,f,e,d,c,b,a : in std_logic;
         S : out std_logic);
end Ejercicio_14;

architecture Behavioral of Ejercicio_14 is

    signal y: std_logic;
begin
    y<= c and (a xnor b) when (d='0') else ((not c) and (b or a)
        or (c and (not b)));


    S<=(not f) and (e xnor g) when (y='0') else f and (e xnor g);

end Behavioral;

```
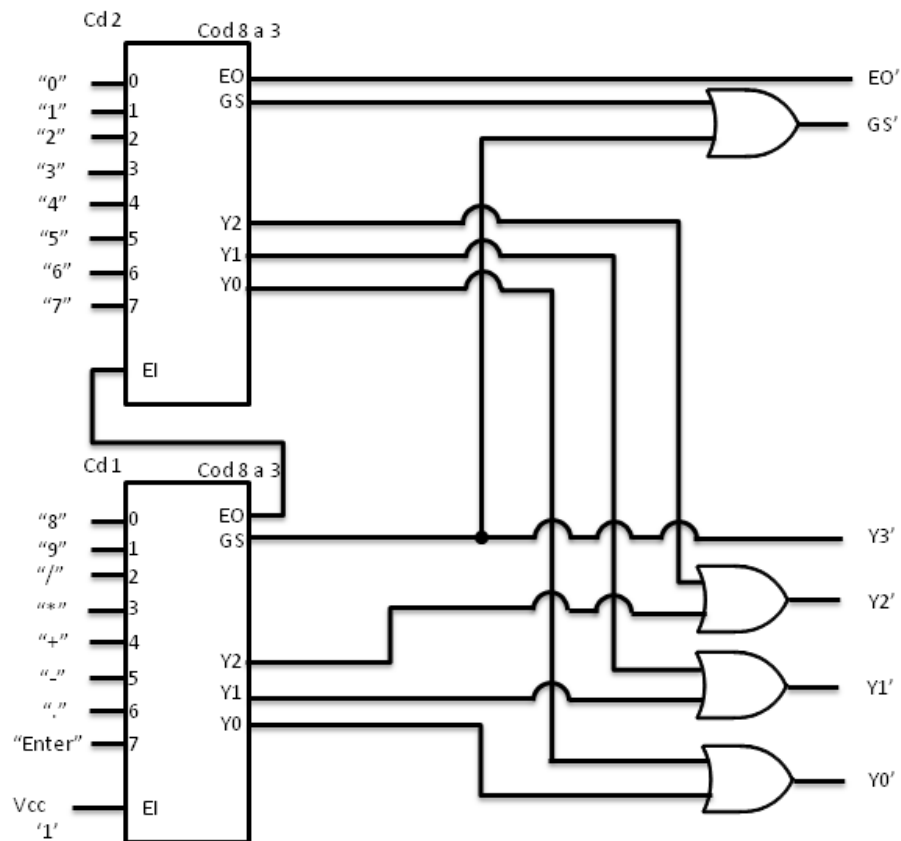
#### Ejercicio 14.

- Si GS='0' no hay ninguna tecla pulsada.
- Si GS='1' hay alguna tecla pulsada.



### Ejercicio 15.

a)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Comparador is
    port(A,B : in std_logic_vector (3 downto 0);
         AmayorB : out std_logic);
end Comparador;

architecture Behavioral of Comparador is
begin
    AmayorB <='1' when A>B else '0';
end Behavioral;
```

b)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Mux2x4 is
    port(D0,D1 : in std_logic_vector (3 downto 0);
         S : in std_logic;
         Y: out std_logic_vector (3 downto 0));
end Mux2x4;

architecture Behavioral of Mux2x4 is
begin
    Y<=D1 when S ='1' else D0;
end Behavioral;
```

c)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Convertidor_BCD_7seg is
    port( N : in std_logic_vector (3 downto 0);
         display: out STD_LOGIC_VECTOR (6 downto 0));
end Convertidor_BCD_7seg;

architecture Behavioral of Convertidor_BCD_7seg is
begin
    with N select
        display<="1111110" when "0000",
                "0110000" when "0001",
                "1101101" when "0010",
                "1111001" when "0011",
                "0110011" when "0100",
                "1011011" when "0101",
                "1011111" when "0110",
                "1110000" when "0111",
                "1111111" when "1000",
                "1111011" when "1001",
                "-----" when others;
end Behavioral;
```

d)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ejercicio16 is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC_VECTOR (3 downto 0);
          display : out STD_LOGIC_VECTOR (6 downto 0));
end ejercicio16;

architecture Behavioral of ejercicio16 is

    Component Comparador
        port(A,B : in std_logic_vector (3 downto 0);
            AmayorB : out std_logic);
    End Component;

    Component Mux2x4
        port(D0,D1 : in std_logic_vector (3 downto 0);
            S : in std_logic;
            Y: out std_logic_vector (3 downto 0));
    End Component;

    Component Convertidor_BCD_7seg
        port( N : in std_logic_vector (3 downto 0);
            display: out STD_LOGIC_VECTOR (6 downto 0));
    End Component;
    signal C1 : std_logic;
    signal C2 : std_logic;
    signal R1 : std_logic_vector (3 downto 0);
    signal R2 : std_logic_vector (3 downto 0);

begin
    U1: Comparador port map (A=>A,B=>B,AmayorB=>C1);
    U2: Mux2x4 port map (D0=>B,D1=>A,S=>C1,Y=>R1);
    U3: Comparador port map (A=>R1,B=>C,AmayorB=>C2);
    U4: Mux2x4 port map (D0=>C,D1=>R1,S=>C2,Y=>R2);
    U5: Convertidor_BCD_7seg port map (N=>R2,display=>display);
end Behavioral;
```