 



Soluciones Tema 4

Ejercicio 1.




Ejercicio 2.

Biastable J-K:

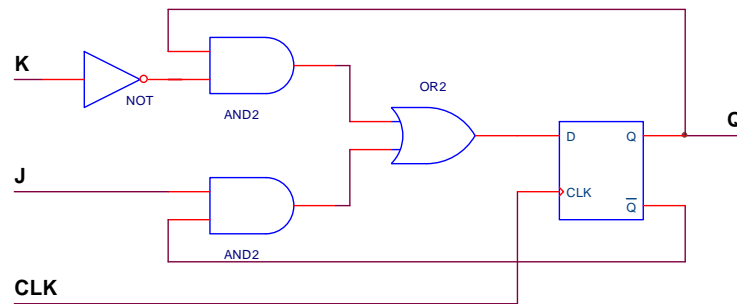


Biastable T:

 


Ejercicio 3.

Biastable T:

 

Biastable D:

 

Ejercicio 4.

-- flipflop_D con entrada de Enable

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity flipflop_D is
    port(CLK,not_CLR,CE,D : in std_logic;
          Q : out std_logic);
end flipflop_D;


architecture Behavioral of flipflop_D is

begin
    process (CLK,not_CLR)
    begin
        if (not_CLR = '0') then Q<='0';
        elsif (CLK'event and clk='1') then
            if (CE='1')then
                Q<=D;
            end if;
        end if;
    end process;


end Behavioral;
```

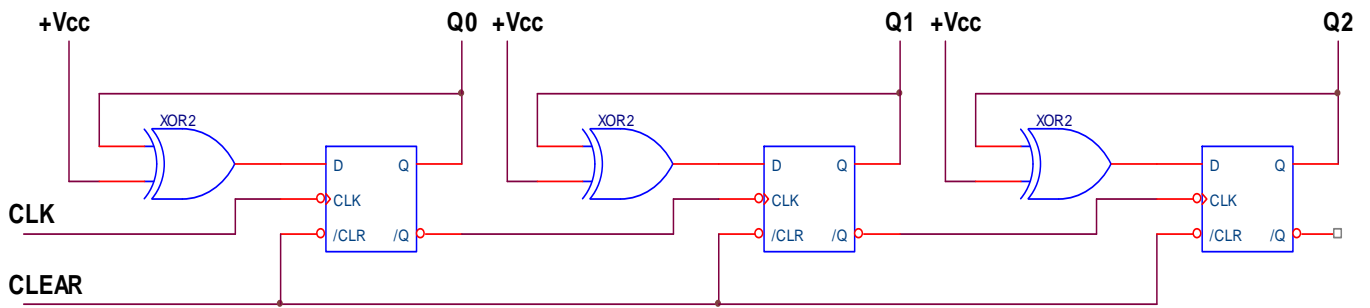Ejercicio 5.

-Contador binario asíncrono descendente de 3 bits (módulo 8).




Solución óptima:

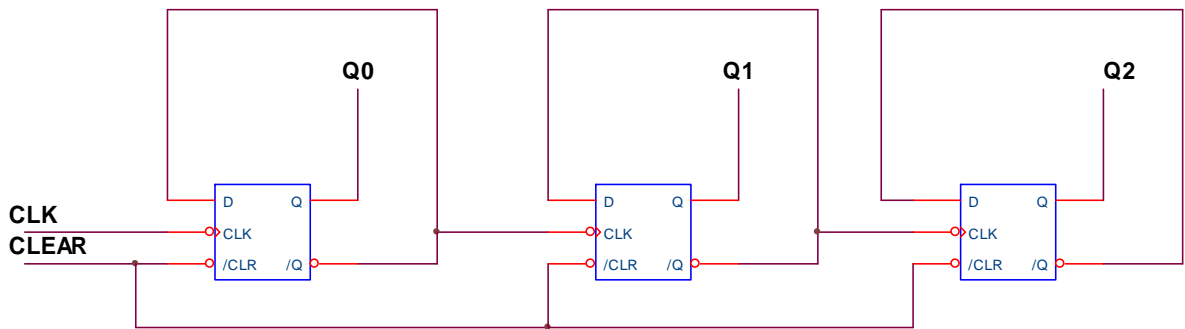

Ejercicio 6.


a)

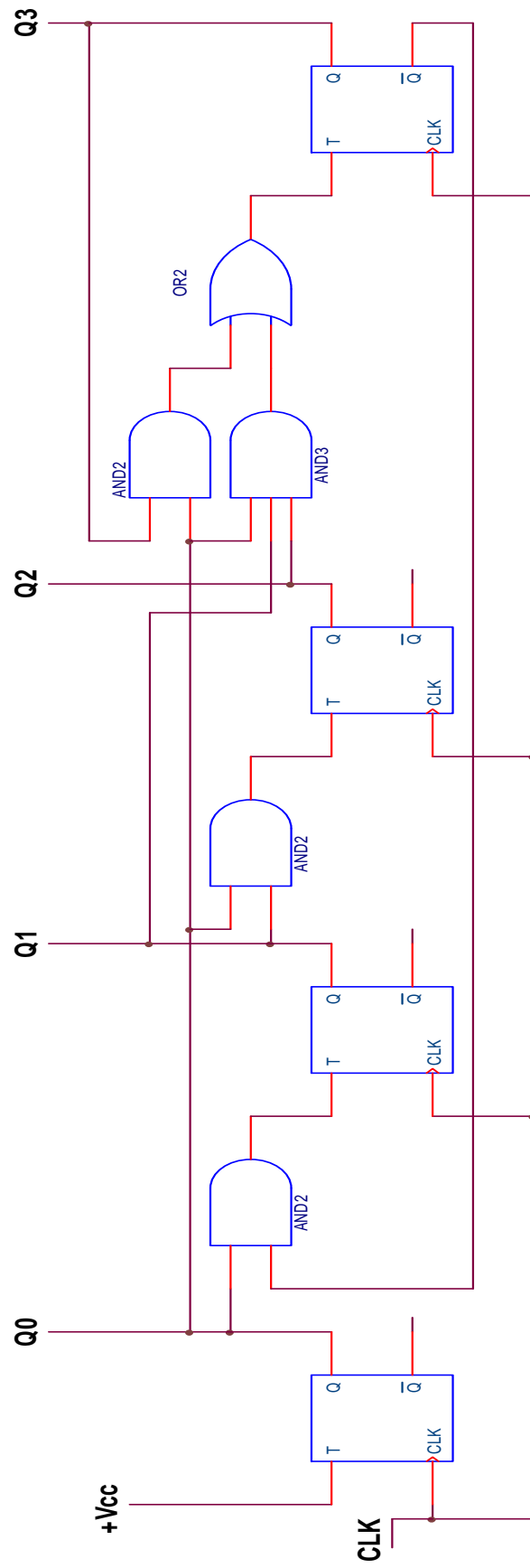


b)

```
-----  
-- Contador síncrono reversible módulo 8  
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
entity Contador_reversible is  
    Port (CLK: in std_logic;  
          Reset: in std_logic;  
          UP: in std_logic;  
          Q: out std_logic_vector (2 downto 0));  
end Contador_reversible;  
  
architecture Behavioral of Contador_reversible is  
    signal cnt_temp :STD_LOGIC_VECTOR (2 downto 0);  
begin  
    process(CLK,Reset)  
    begin  
        if(Reset='1')then  
            cnt_temp<="000";  
        elsif(CLK'event and CLK='1') then  
            if(UP='1') then  
                cnt_temp<=cnt_temp+1;  
            else  
                cnt_temp<=cnt_temp-1;  
            end if;  
        end if;  
    end process;  
    Q<=cnt_temp;  
end Behavioral;
```

Ejercicio 8.

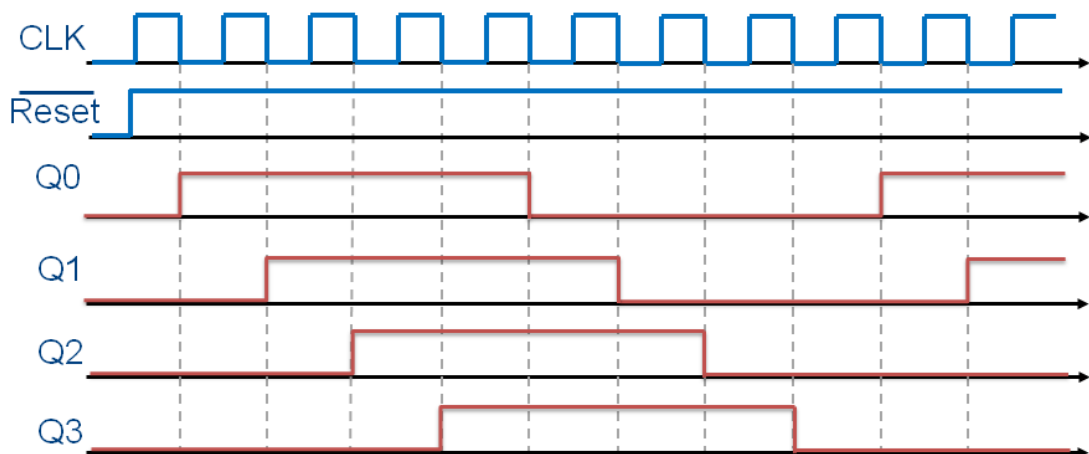

Ejercicio 10.

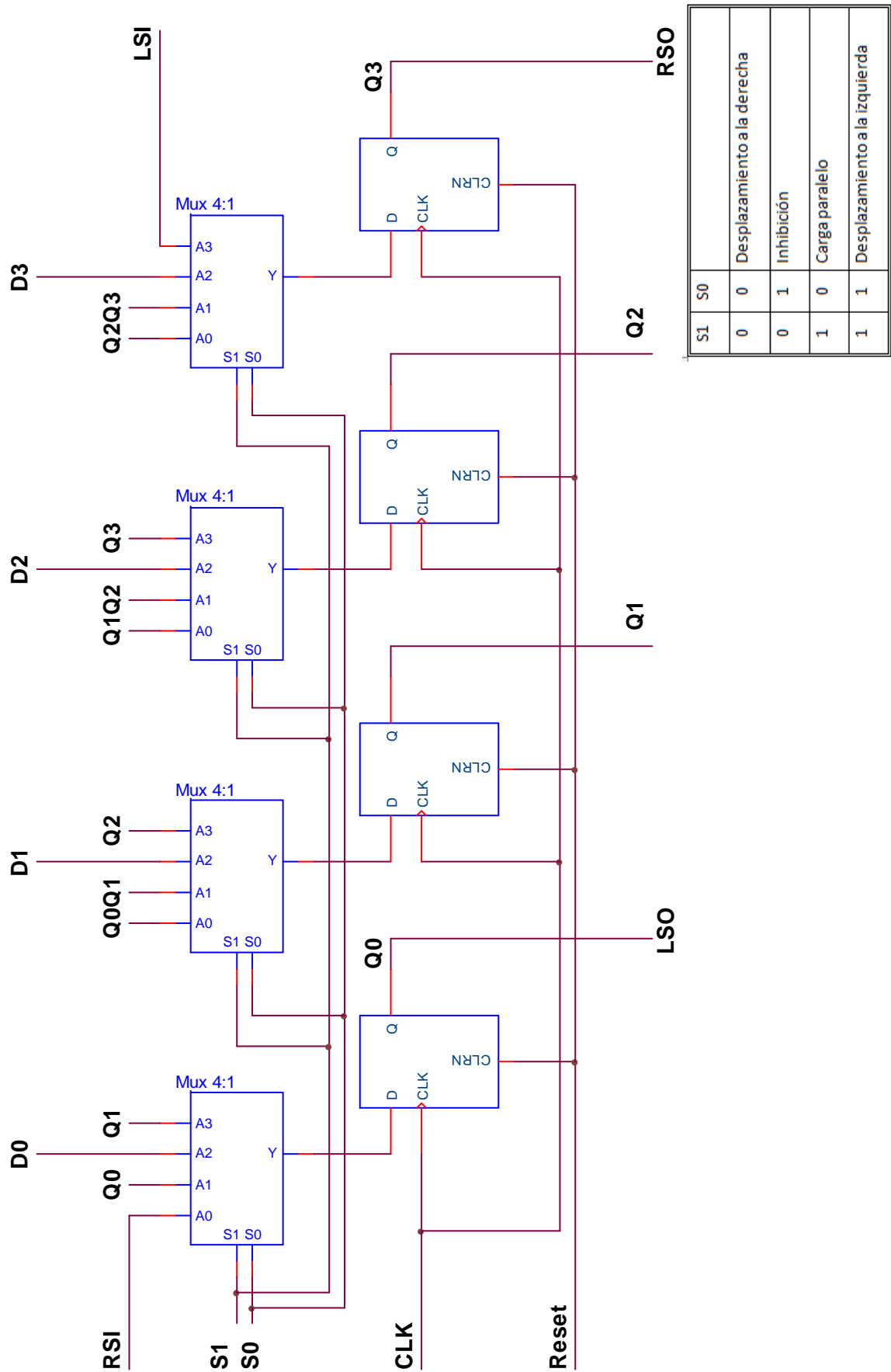

S1	S0	
0	0	Desplazamiento a la derecha
0	1	Inhibición
1	0	Carga paralelo
1	1	Desplazamiento a la izquierda